

Interfacing Display Devices: LED, Seven- Segment Display and LCD

Fundamentos de Microprocesadores y
Microcontroladores P2022

Light Emitting Diodes

When the anode of an LED is made positive with respect to the cathode, it will be forward-biased and will emit the light. The specifications of an LED are its forward voltage V_F and forward current I_F .

The typical values of V_F are from 2 to 3 V and that of I_F are from 10 to 20 mA, depending upon the type and size of the LED. The LEDs are normally operated around I_F .

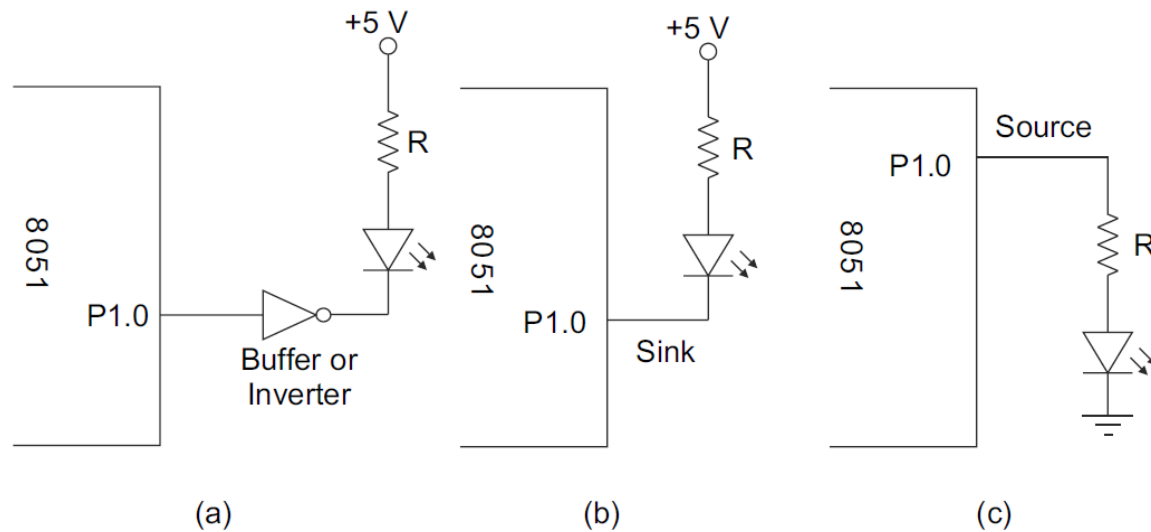


Fig. 18.1 LED interfacing with 8051

The resistor R will limit the current through the LED and protects it from damage. The value of R for a LED having $V_F = 2$ V and $I_F = 10$ mA can be calculated as follows:

$$R = \frac{5 - V_F}{I_F} = \frac{5 - 2}{0.01} = 300 = 330$$

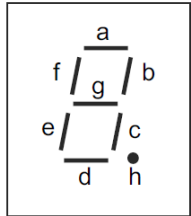


Fig. 18.3 Seven-segment module

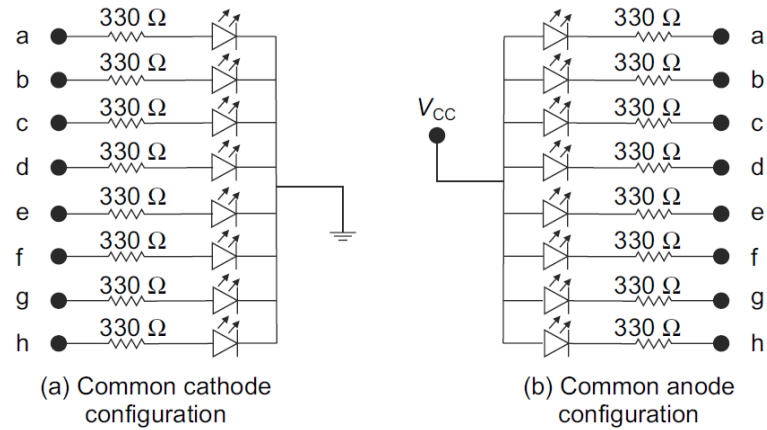


Fig. 18.4 Common cathode and anode configurations

Seven-Segment Display

A seven-segment display is used to display the decimal (or hexadecimal) numbers. They consist of a group of seven LEDs (rectangular), they also have LED for a dot point (decimal point), therefore, they contain eight LEDs in a module which are arranged as shown in Figure 18.3.

The LEDs are assigned names as a to h as shown. Seven-segment displays are used for displaying the numeric information in the electronic meters, digital clocks, and other electronic devices. There are two types of seven-segment display modules: (i) common cathode: where all the LEDs in the module have common cathode and, (ii) common anode: where all the LEDs have common anode.

Digit Multiplexing

When two or more digits are required for an application, we need to use digit multiplexing. In this approach, only one display module (digit) is activated at a time and all the modules are refreshed one by one at a fast rate so that all the display modules appear to be simultaneously active.


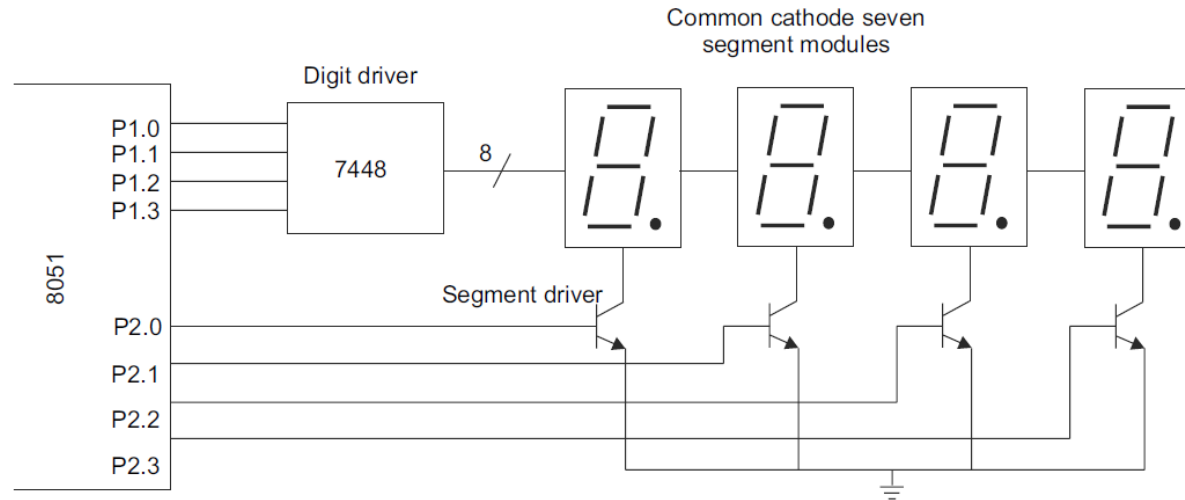


Fig. 18.5 Interfacing four seven-segment common cathode modules with 8051

Digit Multiplexing

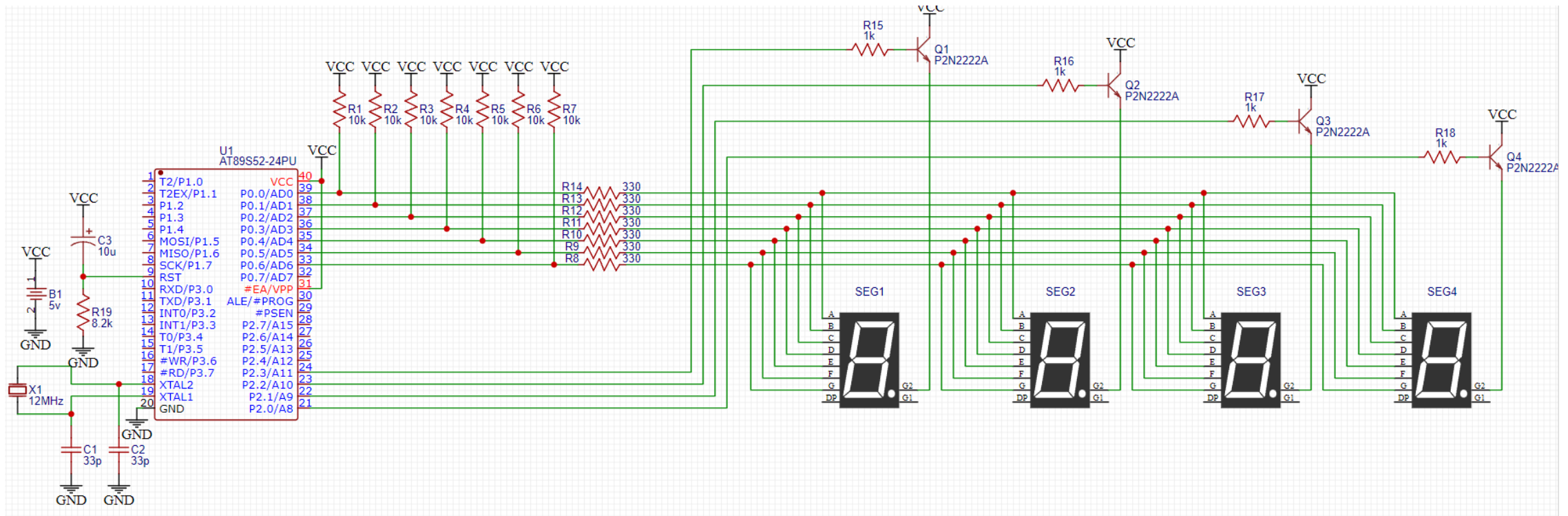

Example

Write a program to display numbers from 0 to 9 repeatedly in a sequence on seven-segment modules.

Solution

```
    ORG 0000h
    MOV DPTR, #0100H
    MOV P2, #0FFH
REPEAT: MOV R0, #00H
NEXT:   MOV A, R0 // display 0 first
        MOVC A, @A+DPTR
        MOV P0, A // send BCD code to 7448
        MOV R5, #200 // delay
```

Solution cont.

```
THERE2: MOV R6, #255
```

```
THERE1: NOP
```

```
    NOP
```

```
    NOP
```

```
    NOP
```

```
    DJNZ R6, THERE1
```

```
    DJNZ R5, THERE2
```

```
    INC R0
```

```
    CJNE R0, #0AH, NEXT // display up to 9 only
```

```
    SJMP REPEAT // repeat the sequence
```


Solution cont.

```
ORG 0100h
```

```
DB 0C0H
```

```
DB 0F9H
```

```
DB 0A4H
```

```
DB 0B0H
```

```
DB 099H
```

```
DB 092H
```

```
DB 082H
```

```
DB 0F8H
```

```
DB 080H
```

```
DB 090H
```

```
END
```

Manish K Patel (2014). *The 8051 Microcontroller Based Embedded Systems*. McGraw Hill Education

References